SignedMultiplier_16bit

Xinyi Ou
Sean Crowley

#Assign named wires to inputs and low

#This column calculates partial products   #This column adds partial products together

#Add 1 for signed multiplier logic

#Inverted partial product inside this subcircuit
for signed multiplier logic

#Add 1 for signed multiplier logic

#Check that highest bit of LOW matches all bits of HIGH,
else overflow occurs